

# CPU Datapath And Control II

Instructor: Dmitri A. Gusev

Fall 2007

CS 502: Computers and Communications

Lecture 7, September 26, 2007

# Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18

Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct

- ALU's operation based on instruction type and function code

# Control (cont'd)

- e.g., what should the ALU do with this instruction
- Example: lw \$1, 100(\$2)

35	2	1	100
----	---	---	-----

op	rs	rt	16 bit offset
----	----	----	---------------

- ALU control input

```
0000  AND
0001  OR
0010  add
0110  subtract
0111  set-on-less-than
1100  NOR
```

- Why is the code for subtract 0110 and not 0011?

# Control

- Must describe hardware to compute 4-bit ALU control input


- given instruction type

00 = lw, sw

01 = beq,

10 = arithmetic

- function code for arithmetic

 


**ALUOp  
computed from instruction type**

- Describe it using a truth table (can turn into gates):

ALUOp		Func field						Operation
ALUOp <sub>1</sub>	ALUOp <sub>0</sub>	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111



**FIGURE 5.13 The truth table for the three ALU control bits (called Operation).** The inputs are the ALUOp and function code field. Only the entries for which the ALU control is asserted are shown. Some don't-care entries have been added. For example, the ALUOp does not use the encoding 11, so the truth table can contain entries 1X and X1, rather than 10 and 01. Also, when the function field is used, the first two bits (F5 and F4) of these instructions are always 10, so they are don't-care terms and are replaced with XX in the truth table.

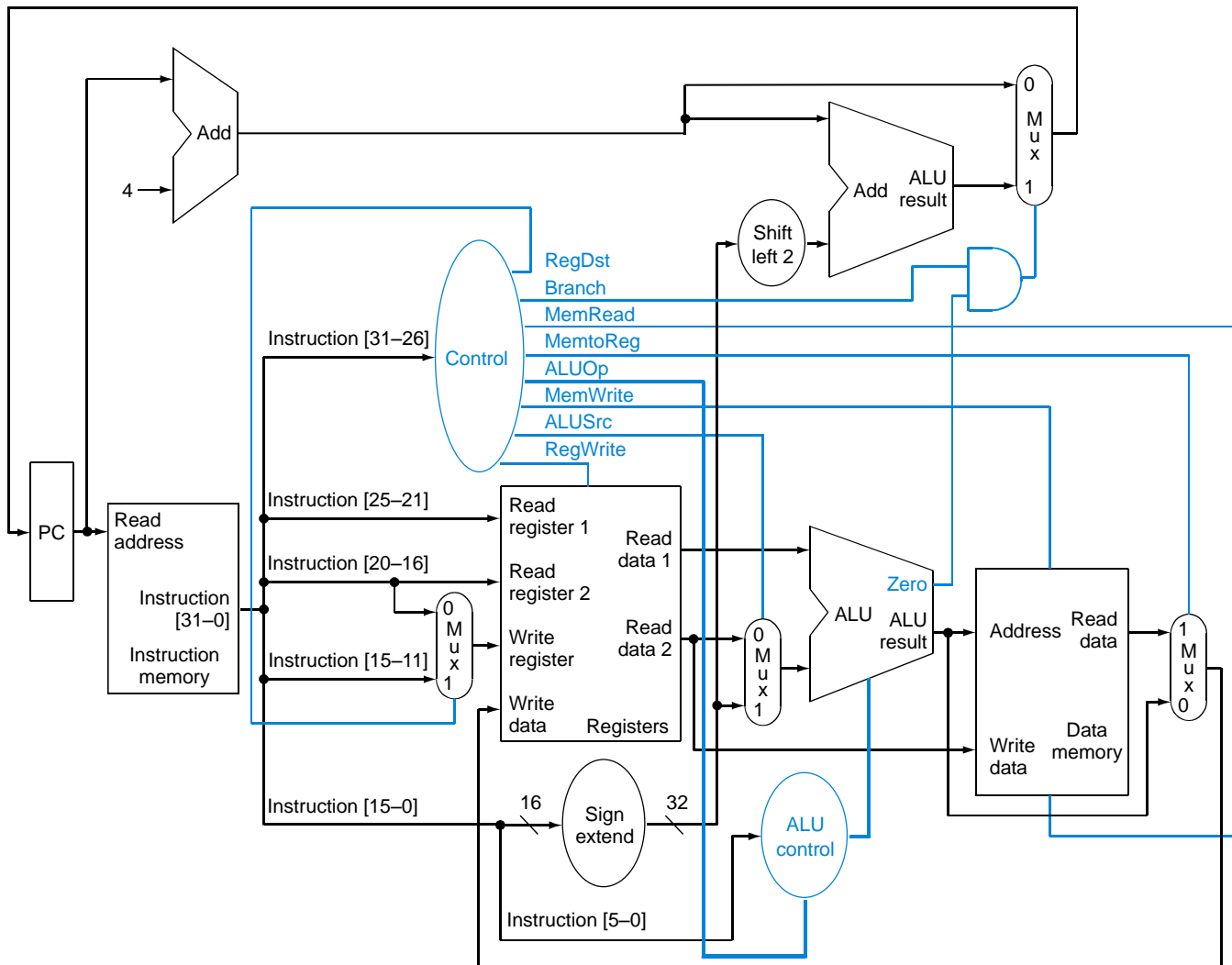

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

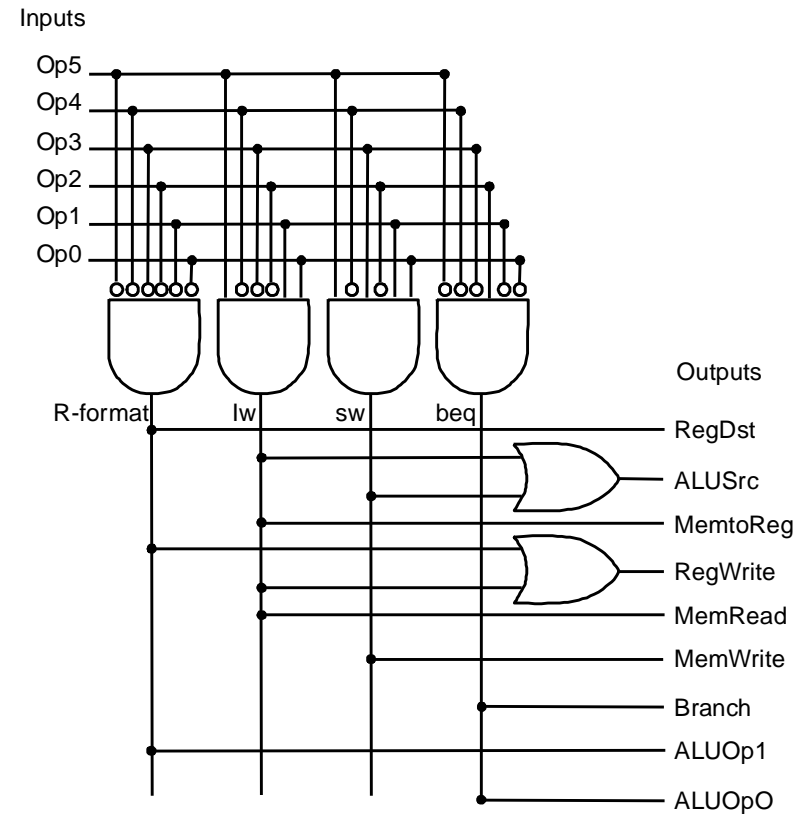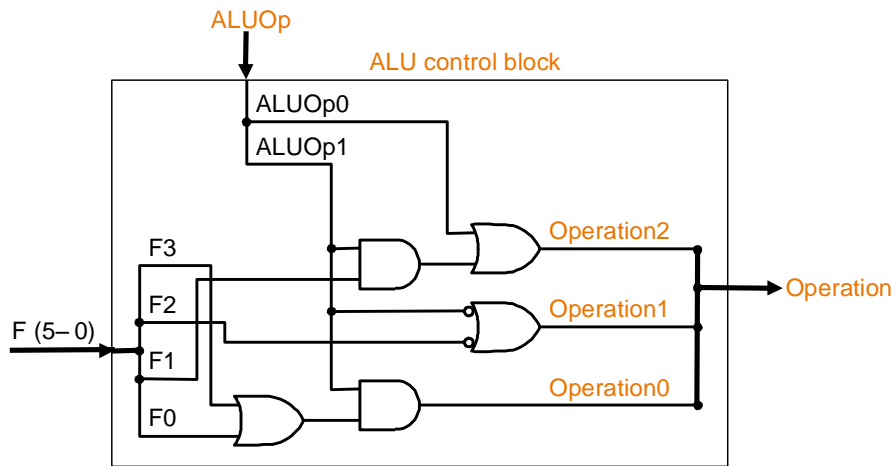
# Control (cont'd)

- Simple combinational logic (truth tables)


 
# Our Simple Control Structure


- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
  - ALU might not produce “right answer” right away
  - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path



***We are ignoring some details like setup and hold times***
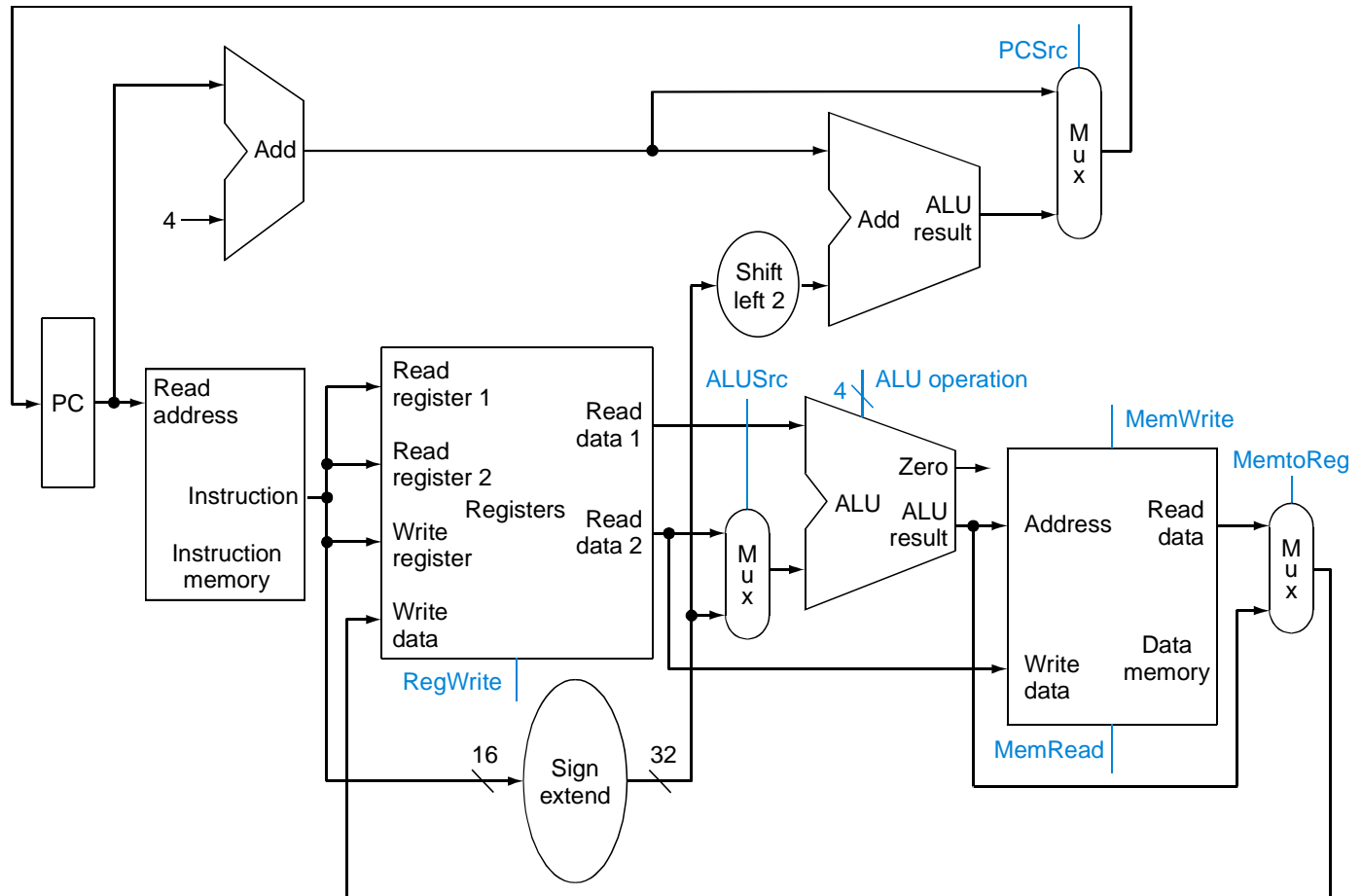
# Single Cycle Implementation


- Calculate cycle time assuming negligible delays except:
  - memory (200ps),
  - ALU and adders (100ps),
  - register file access (50ps)




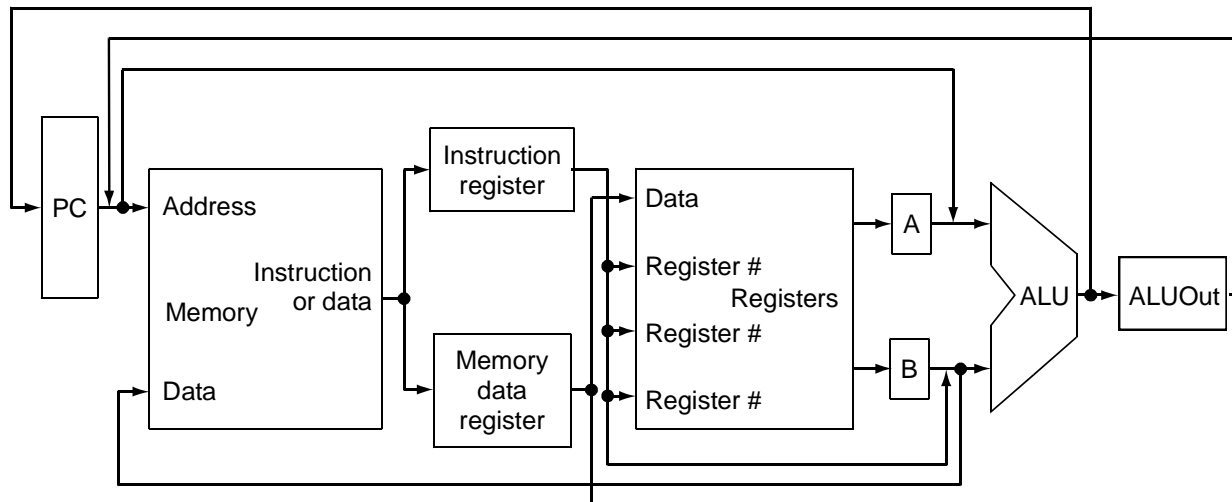
# Where we are headed

- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point?
  - wasteful of area
- One Solution:
  - use a “smaller” cycle time
  - **have different instructions take different numbers of cycles**
  - a “multicycle” datapath:




# Multicycle Approach

- We will be reusing functional units
  - ALU used to compute address and to increment PC
  - Memory used for instruction and data
- Our control signals will not be determined directly by instruction
  - e.g., what should the ALU do for a “subtract” instruction?
- We’ll use a finite state machine for control
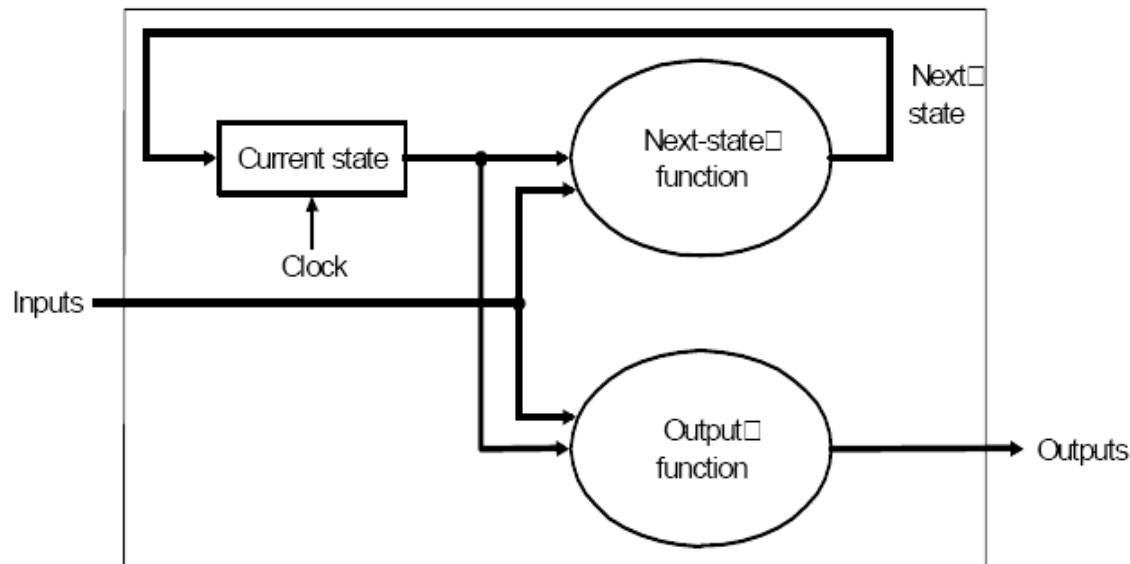
# Finite state machines

---


- **Finite state machines:**
  - a set of states and
  - next state function (determined by current state and the input)
  - output function (determined by current state and possibly input)



- We'll use a Moore machine (output based only on current state)
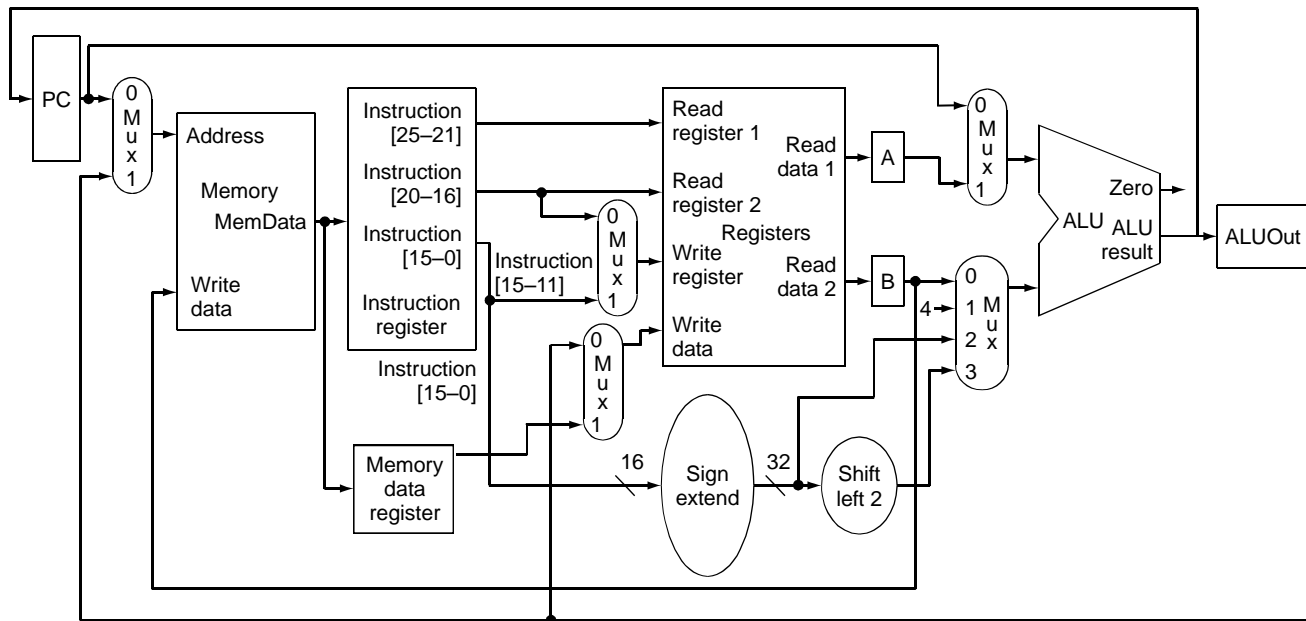
# Multicycle Approach

- Break up the instructions into steps, each step takes a cycle
  - balance the amount of work to be done
  - restrict each cycle to use only one major functional unit
- At the end of a cycle
  - store values for use in later cycles (easiest thing to do)
  - introduce additional “internal” registers



# Five Execution Steps

- Instruction Fetch
- Instruction Decode and Register Fetch
- Execution, Memory Address Computation, or Branch Completion
- Memory Access or R-type instruction completion
- Write-back step

*INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!*

# Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR <= Memory[PC];  
PC <= PC + 4;
```

*Can we figure out the values of the control signals?*

*What is the advantage of updating the PC now?*

# Step 2: Instruction Decode and Register Fetch

- Read registers `rs` and `rt` in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:

```
A <= Reg[IR[25:21]];
B <= Reg[IR[20:16]];
ALUOut <= PC + (sign-extend(IR[15:0])
<< 2);
```

- We aren't setting any control lines based on the instruction type  
(we are busy "decoding" it in our control logic)

# Step 3 (instruction dependent)

- ALU is performing one of three functions, based on instruction type
- Memory Reference:

```
ALUOut <= A + sign-extend(IR[15:0]);
```

- R-type:

```
ALUOut <= A op B;
```

- Branch:

```
if (A==B) PC <= ALUOut;
```



# Step 4 (R-type or memory-access)

- Loads and stores access memory

```
MDR <= Memory[ALUOut];  
    or  
Memory[ALUOut] <= B;
```

- R-type instructions finish

```
Reg[IR[15:11]] <= ALUOut;
```

*The write actually takes place at the end of the cycle on the edge*

# Write-back step

- $\text{Reg}[\text{IR}[20:16]] \leftarrow \text{MDR};$

*Which instruction needs this?*

# Summary:


Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR \leftarrow \text{Memory}[PC]$ $PC \leftarrow PC + 4$			
Instruction decode/register fetch	$A \leftarrow \text{Reg} [IR[25:21]]$ $B \leftarrow \text{Reg} [IR[20:16]]$ $ALUOut \leftarrow PC + (\text{sign-extend} (IR[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut \leftarrow A \text{ op } B$	$ALUOut \leftarrow A + \text{sign-extend} (IR[15:0])$	If (A == B) $PC \leftarrow ALUOut$	$PC \leftarrow \{PC [31:28], (IR[25:0], 2'b00)\}$
Memory access or R-type completion	$\text{Reg} [IR[15:11]] \leftarrow ALUOut$	Load: $MDR \leftarrow \text{Memory}[ALUOut]$ or Store: $\text{Memory} [ALUOut] \leftarrow B$		
Memory read completion		Load: $\text{Reg}[IR[20:16]] \leftarrow MDR$		

**FIGURE 5.30 Summary of the steps taken to execute any instruction class.** Instructions take from three to five execution steps. The first two steps are independent of the instruction class. After these steps, an instruction takes from one to three more cycles to complete, depending on the instruction class. The empty entries for the Memory access step or the Memory read completion step indicate that the particular instruction class takes fewer cycles. In a multicycle implementation, a new instruction will be started as soon as the current instruction completes, so these cycles are not idle or wasted. As mentioned earlier, the register file actually reads every cycle, but as long as the IR does not change, the values read from the register file are identical. In particular, the value read into register B during the Instruction decode stage, for a branch or R-type instruction, is the same as the value stored into B during the Execution stage and then used in the Memory access stage for a store word instruction.

# Implementing the Control

- Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
- Use the information we've accumulated to specify a finite state machine
  - specify the finite state machine graphically, or
  - use microprogramming
- Implementation can be derived from specification

# Graphical Specification of FSM

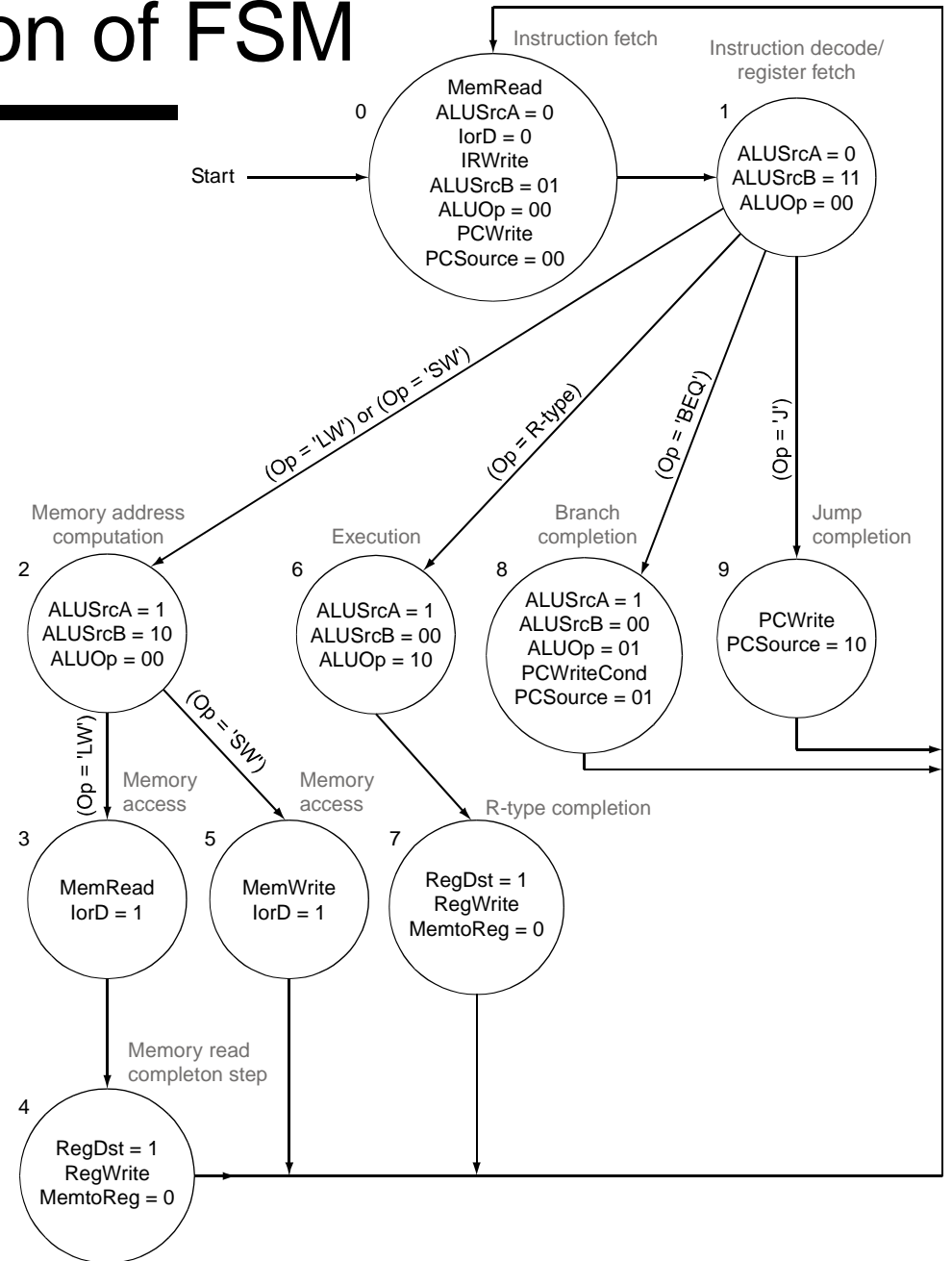

# Chapter 5 Summary

- If we understand the instructions...
  - We can design a simple processor!
- If instructions take different amounts of time, the multi-cycle approach is better
- Datapath implemented using:
  - Combinational logic for arithmetic
  - State holding elements to remember bits
- Control implemented using:
  - Combinational logic for single-cycle implementation
  - Finite state machine for multi-cycle implementation