
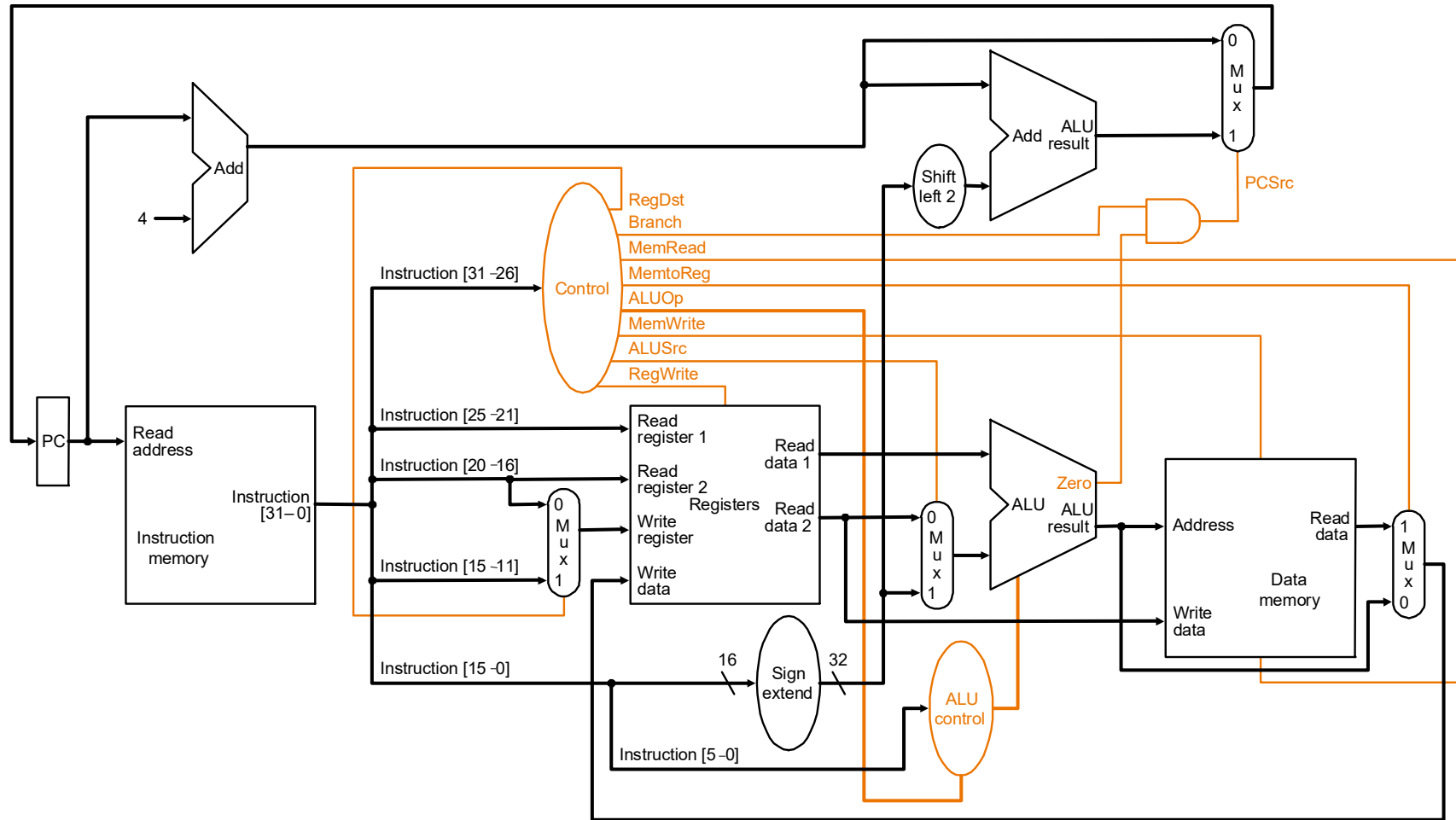


 Our ultimate goal: building the MIPS datapath





Arithmetic Logic Unit (ALU)



ALU operation (2-bit):


- 00 = and
- 01 = or
- 10 = add

 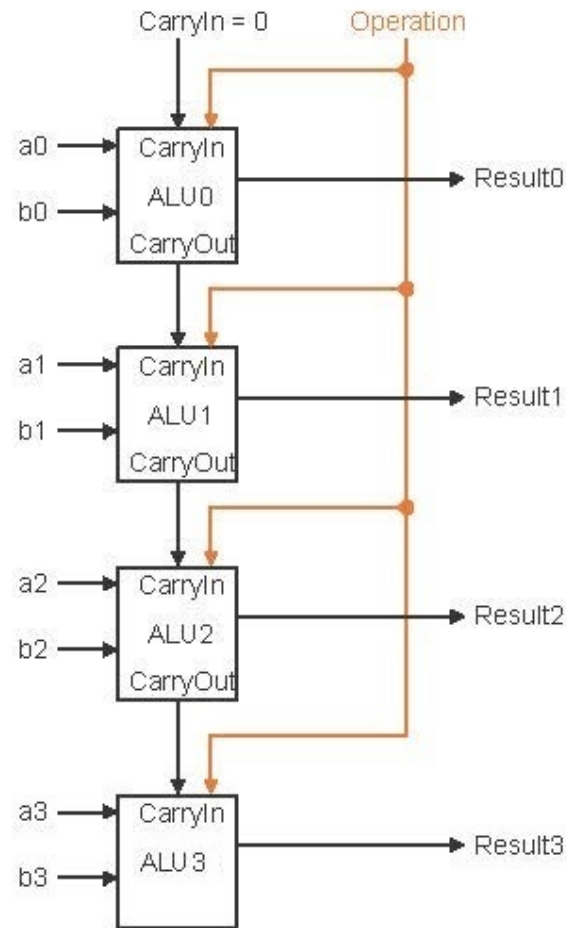


What about subtraction $(a - b)$?

- Two's complement approach: just negate b and add.
- How do we negate?

Invert all bits of b

 

Add 1

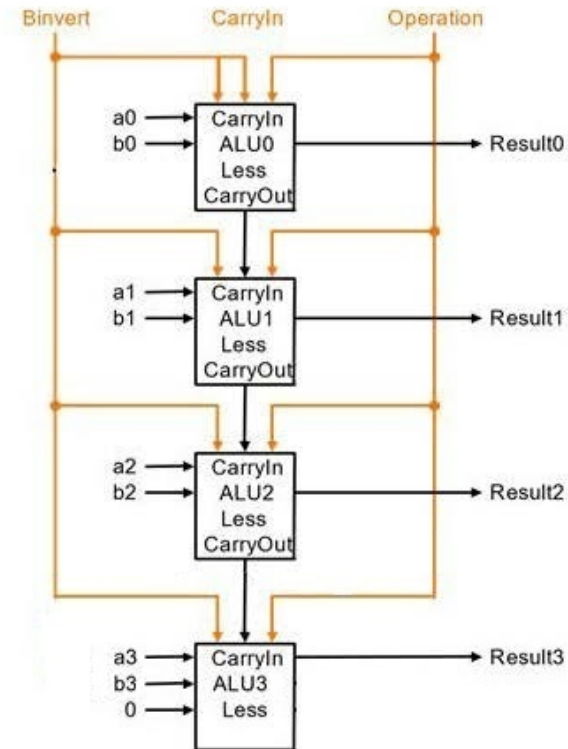

ALU operation (3-bit):

Binvert	Operation	
0	00	= and
0	01	= or
0	10	= add
1	10	= sub

Tailoring the ALU to the MIPS datapath

- Need to support the set-on-less-than instruction


```
slt rd, rs, rt
```

- slt is an arithmetic instruction
- produces a 1 if $rs < rt$ and 0 otherwise
- use subtraction: $(a-b) < 0$ implies $a < b$

- Need to support test for equality (beq \$t5, \$t6, label)

- use subtraction: $(a-b) = 0$ implies $a = b \Rightarrow \text{Zero}=1$

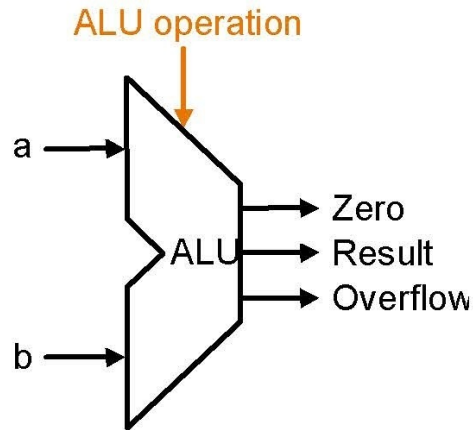Test for equality and complete ALU (3-bit control)




ALU operation:

000 = and
 001 = or
 010 = add
 110 = subtract
 111 = slt




Control lines

Bnegate	Operation	Instruction
0	00	and
0	01	or
0	10	add
1	10	sub
1	11	slt

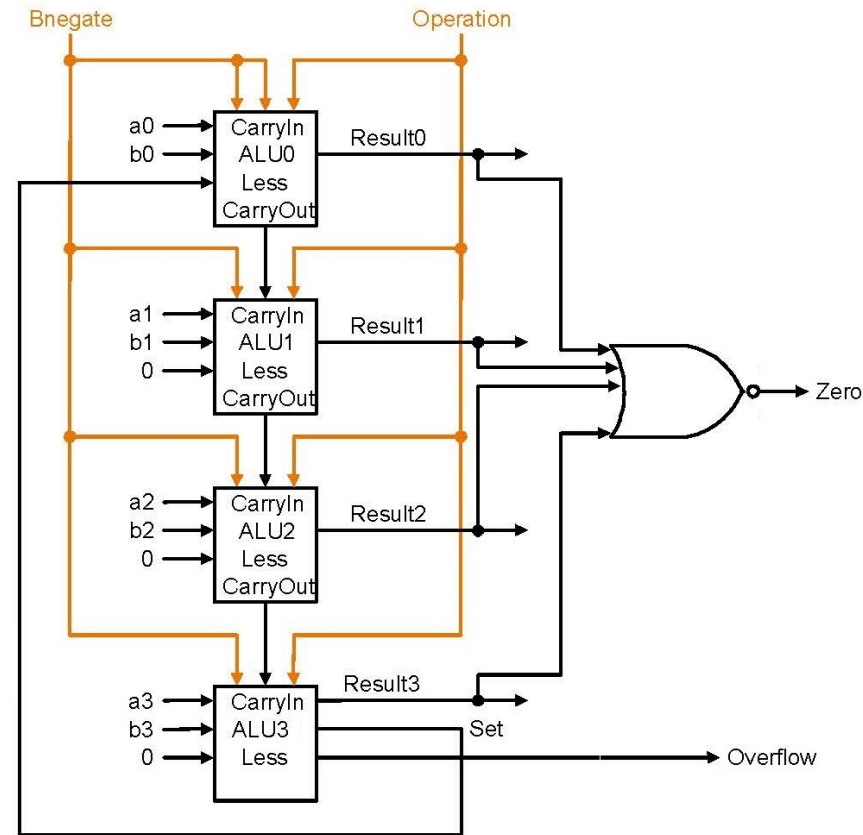

• Note: zero is a 1 when the result is zero!

Adding NOR and NAND operations

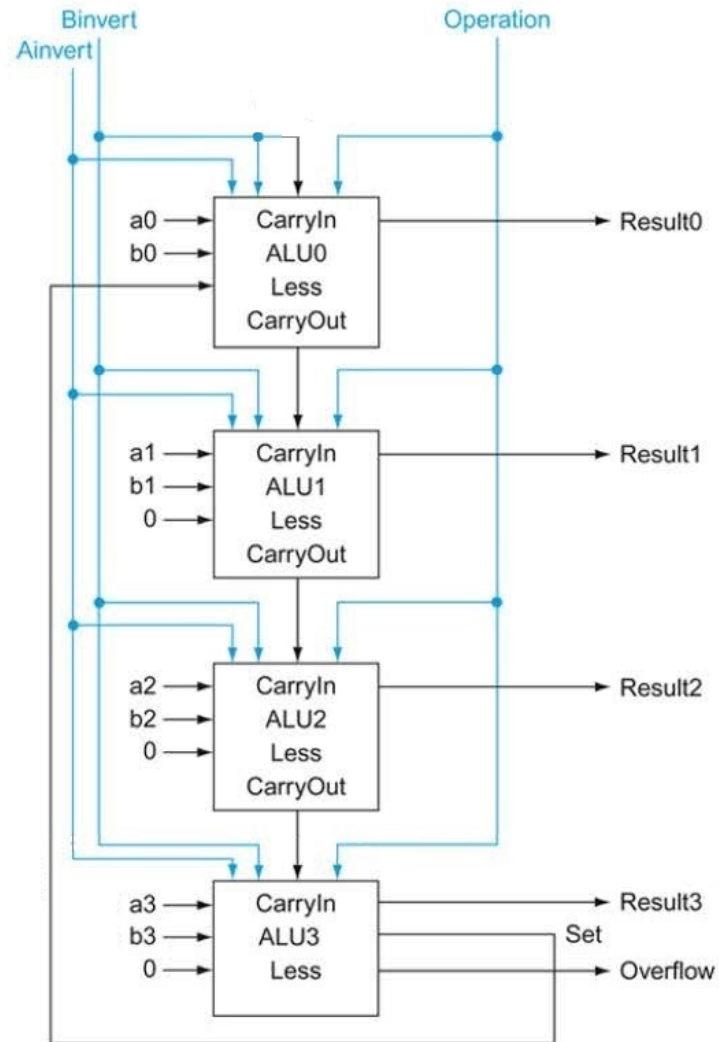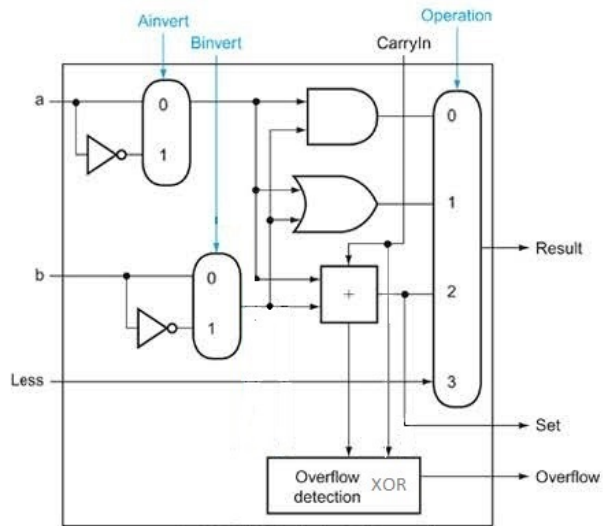 

Final ALU (4-bit control)

ALU Control lines

Ainvert	Bnegate	Operation	Instruction
0	0	00	and
0	0	01	or
0	0	10	add
0	1	10	sub
0	1	11	slt
1	1	00	nor
1	1	01	nand

