

## The Processor: Datapath & Control


---

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
  - memory-reference instructions: `lw`, `sw`
  - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
  - control flow instructions: `beq`, `j`
- Generic Implementation:
  - use the program counter (PC) to supply instruction address
  - get the instruction from memory
  - read registers
  - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
  - Why? memory-reference? arithmetic? control flow?

## More Implementation Details

---


- Abstract / Simplified View:

 


Two types of functional units:

- elements that operate on data values (combinational)
- elements that contain state (sequential)

# Major components

 


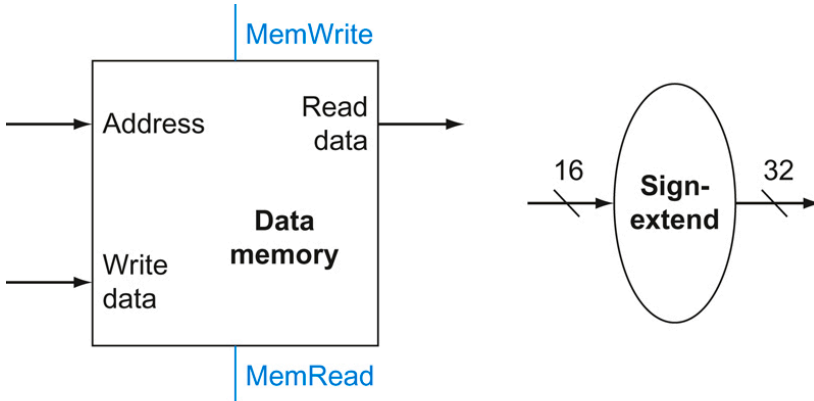Copyright © 2021 Elsevier Inc. All rights reserved




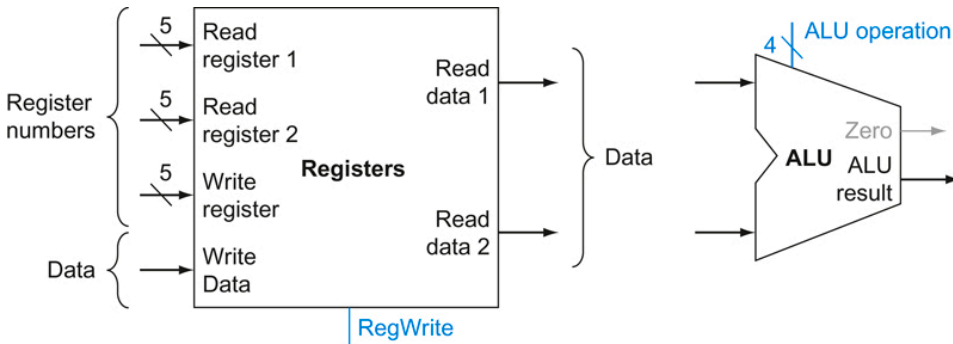
a. Data memory unit      b. Sign extension unit

Copyright © 2021 Elsevier Inc. All rights reserved



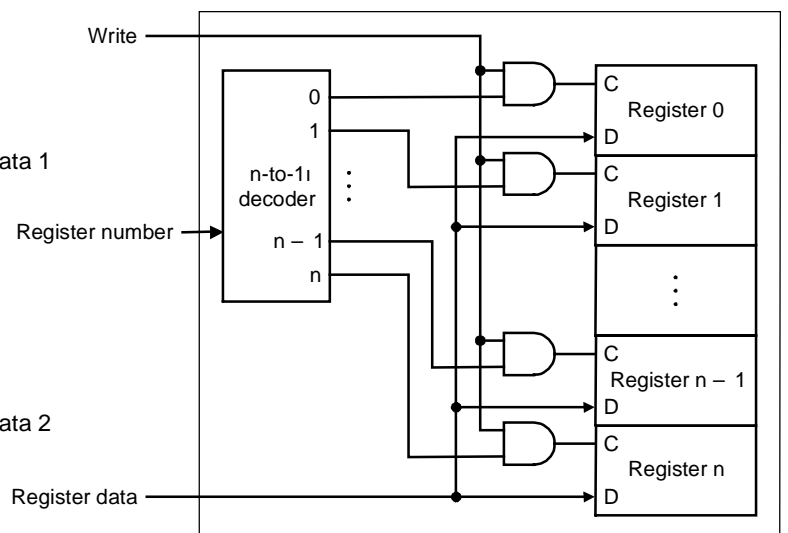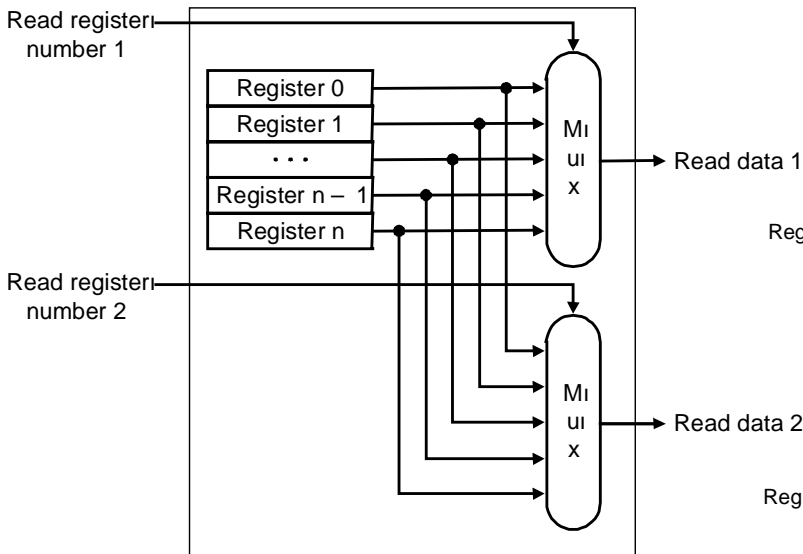a. Registers      b. ALU


Copyright © 2021 Elsevier Inc. All rights reserved



## D flip-flop

---


- Output changes only on the clock edge

 

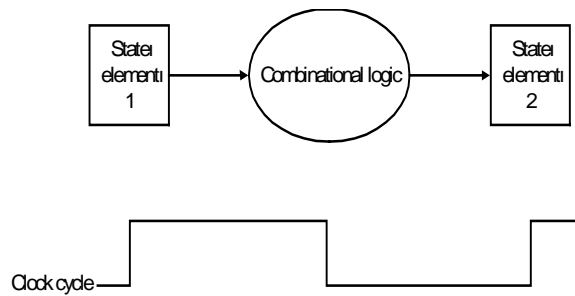
## Our Implementation

---


- An edge triggered methodology
- Typical execution:
  - read contents of some state elements,
  - send values through some combinational logic
  - write results to one or more state elements



 
## Fetching instructions and incrementing PC




## Datapath for R-type instructions

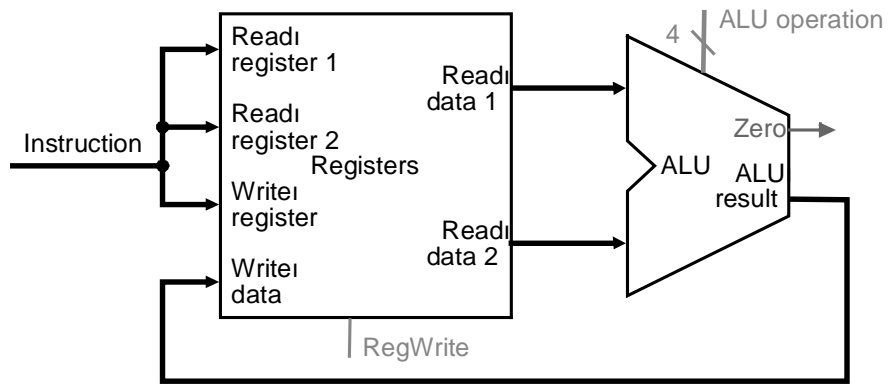


## Datapath for load and store

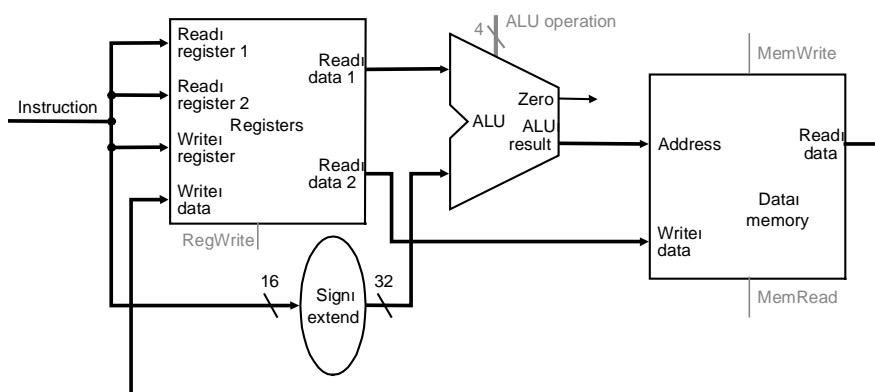


## Datapath for branching instructions

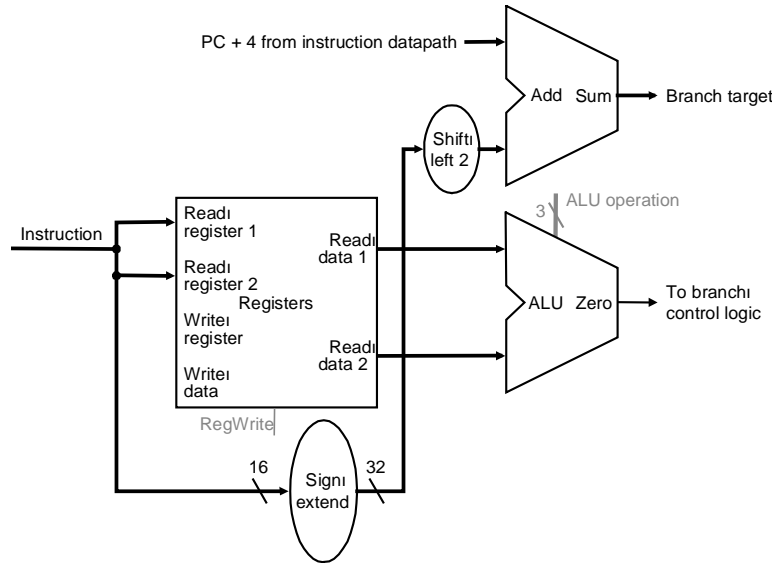

## Building the Datapath

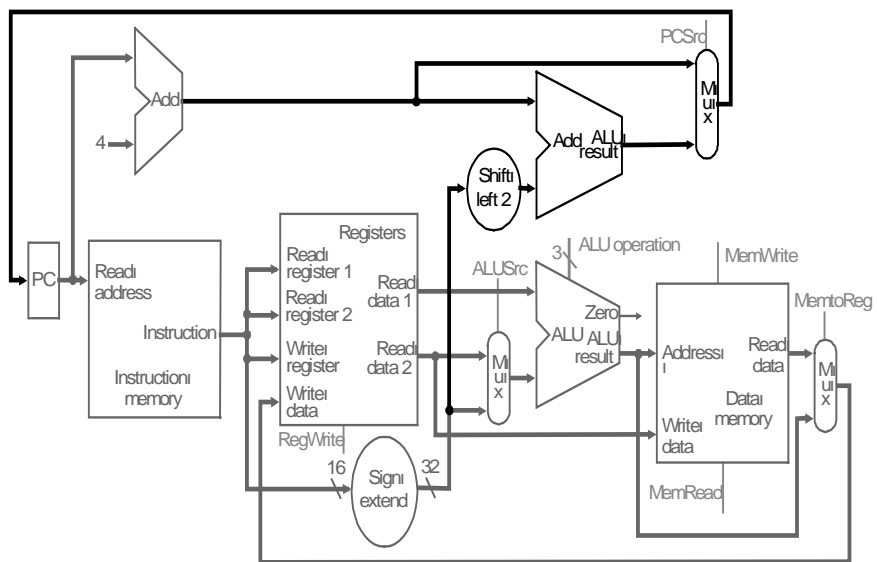

# Complete Datapath

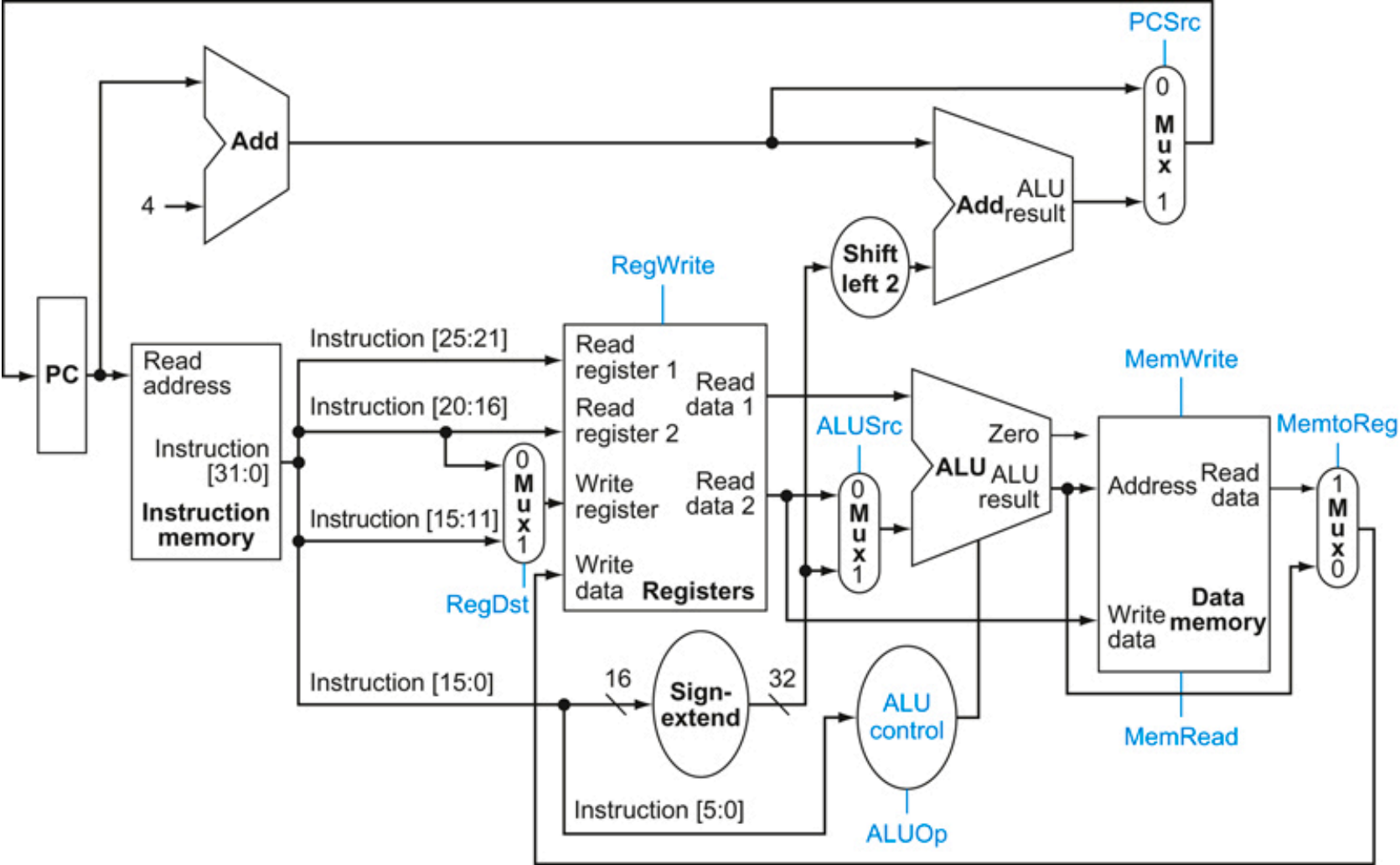

Copyright © 2021 Elsevier Inc. All rights reserved